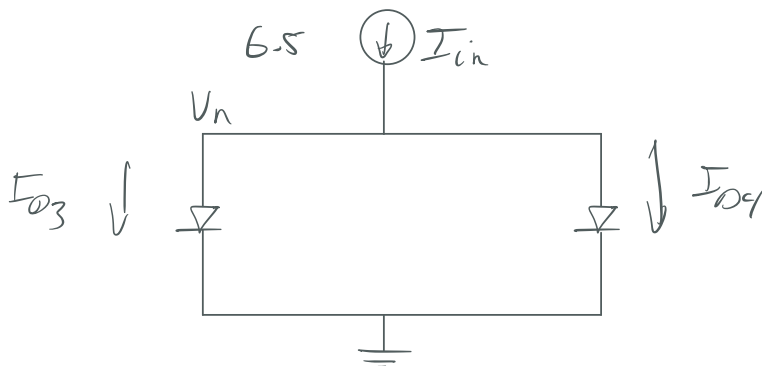


i)



$$I_{S3} = 2.45 \times 10^{-13}$$

$$I_{S4} = 8.37 \times 10^{-13}$$

Find : V_n , I_{D3} , I_{D4}


Solution:

$$I_d = I_s e^{V_d/V_t}$$

$$V_t = 25 \text{ mV}$$

$$V_d = V_n = ?$$

ii) Find V_n

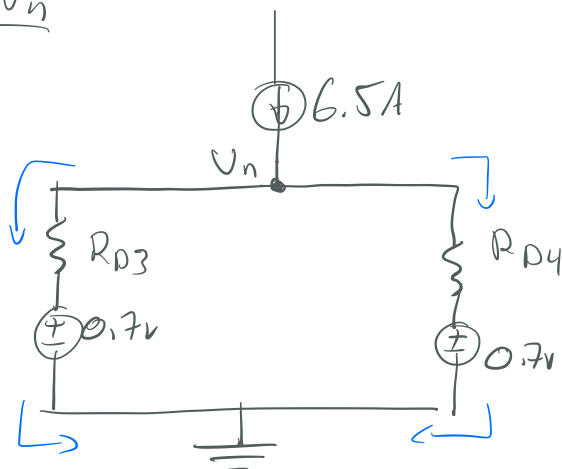

$$R_{D3} = \frac{V_T}{I_{D3}}$$

$$R_{D4} = \frac{V_T}{I_{D4}}$$

$$0.7 - V_n + 0.7 - V_n = 6.5$$

$$I_{D3} + I_{D4} = 6.5$$

$$(2.45 \times 10^{-13}) e^{V_n/0.025} + (8.37 \times 10^{-13}) e^{V_n/0.025} = 6.5$$

$$6.5 = (2.45 + 8.37) 10^{-13} \cdot e^{V_D/0.025}$$

$$e^{V_D/0.025} = \frac{6.5}{10.82 \times 10^{-13}}$$

$$\ln(e^{V_D/0.025}) = (6.007393715 \times 10^{12})$$

$$V_D = 0.025 \ln(6.007393715 \times 10^{12})$$


$$\textcircled{1} \quad V_D = 0.7356 \text{ V} \quad d$$

$$\textcircled{2} \quad I_{D3} = (2.45 \times 10^{-13}) e^{0.7356/0.025} = 1.47179 \text{ A} \quad e$$

$$\textcircled{3} \quad I_{D4} = (8.37 \times 10^{-13}) e^{0.7356/0.025} = 5.028127 \text{ A} \quad b$$

2)

①

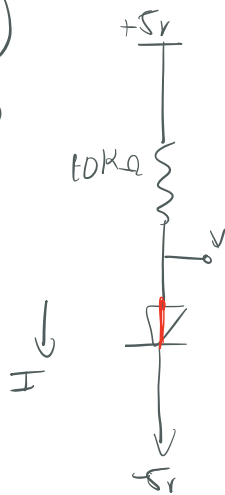

①

KVL

$$5 - I(10K) - 0.67 = -5$$

$$+ I(10K) = +9.33$$


$$I = \frac{9.33}{10K}$$

$$I = .933 \text{ mA}$$


$$V = 0.67 - 5$$

$$V = -4.33 \text{ V}$$

②

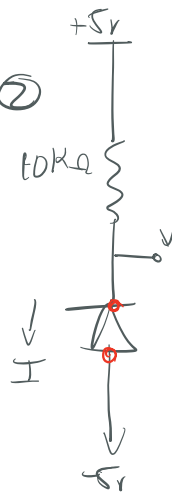

③

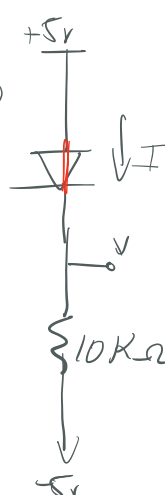

④



$$P = (4.33)(.933 \text{ mA}) = \underline{4.03989 \text{ mW}}$$

$$\textcircled{2} \quad I=0 \quad V=5, \quad P = (5)^2 / 10K = \underline{2.5 \text{ mW}}$$

$$\textcircled{3} \quad 5 - 0.67 - I(10K) = -5$$

$$I(10K) = 9.33$$

$$I = .933 \text{ mA}$$

$$V = 5 - 0.67$$

$$V = \underline{4.33 \text{ V}}$$

$$P = IV = (.933 \text{ mA})(4.33) = \underline{4.0389 \text{ mW}}$$

④) $I=0$ $V=-5$ $p = (-5)^2 / 10k = \underline{2.5mW}$


Conclusion

3) A shunt regulator utilizing a zener diode with an incremental resistance of 10Ω is fed through a 200Ω resistor. What is the regulator's output if raw supply changes by $1.4V$

$$\frac{\Delta V_o}{\Delta V_s} = \frac{10}{10+200} = 0.0476190476$$


$$\Delta V_s = 1.4V$$
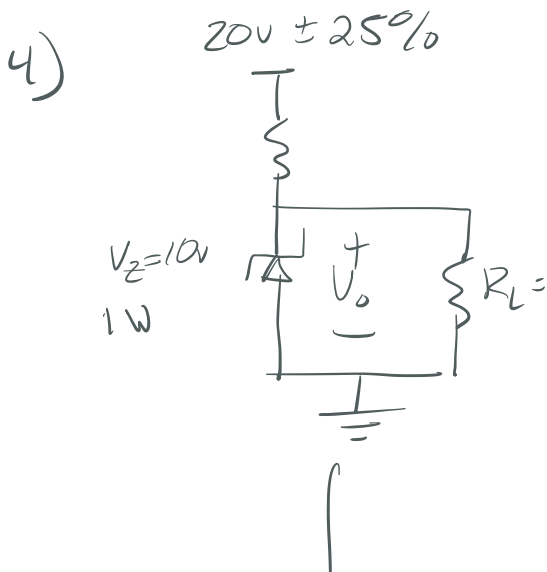
$$\Delta V_o = 0.047619 \cdot \Delta V \Rightarrow 0.047619 \cdot 1.4 = \underline{66.667mV_a}$$



$$I_T = 25mA$$

$$r_z = 18\Omega$$

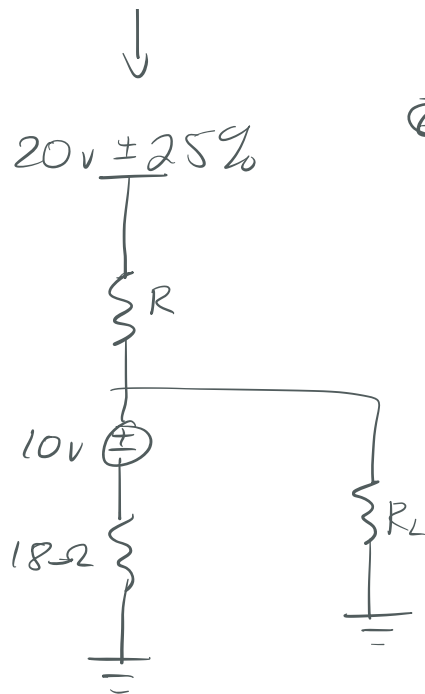

⑥

$$V_{ZT} = V_{Z0} + r_z I_{ZT}$$

$$V_{Z0} = V_{ZT} - r_z I_{ZT}$$

$$V_{Z0} = 10 - 18(25 \text{ mA})$$


$$V_{Z0} = 9.55 \text{ V}$$

⑦

Max current = 20 mA

$$I_z(\text{max}) = \underline{20 \text{ mA}}, \quad I_z(\text{min}) = \underline{5 \text{ mA}}$$
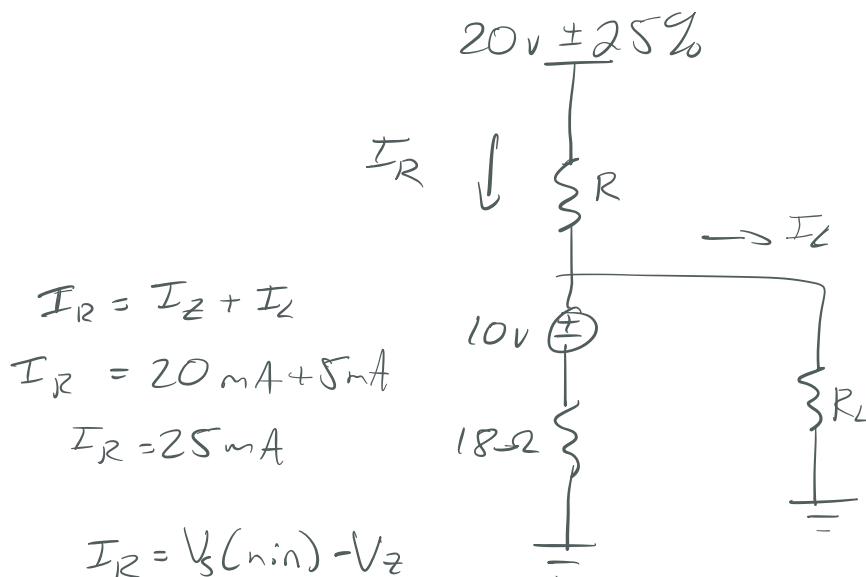
$$V_s(\text{min}) = 20 - 25\%(20) = \underline{15 \text{ V}}$$



$$I_R = I_Z + I_S$$

$$I_R = 20 \text{ mA} + 5 \text{ mA}$$

$$I_R = 25 \text{ mA}$$

$$I_R = \frac{V_s(\text{min}) - V_Z}{R}$$

$$R = \frac{V_s - (V_{Z0} + r_z I_Z)}{I_R}$$

$$R = \frac{15 - (9.55 + 18(5\text{mA}))}{25\text{mA}} \Rightarrow R = 214.4 \Omega$$

$$\textcircled{8} \quad \frac{\Delta V_o}{\Delta V^+} = \frac{r_z}{R + r_z} = \frac{18}{214.4 + 18} = 0.07745266\% \times 100\%$$

$$\text{line reg} = 7.745266\% \text{ (d)}$$

⑨ Load regulation

$$\frac{\Delta V_o}{\Delta I_L} = -(r_z || R)$$

$$\frac{\Delta V_o}{\Delta I_L} = -\frac{r_z R}{R_z + R} = \frac{18(214.4)}{18 + 214.4} = -16.605$$

$$\frac{\Delta V_o}{\Delta I_L} = -16.05$$

$$\Delta V_o = -16.05 \Delta I_L$$

$$\Delta V_o = -16.05(25\text{mA}) \quad \Delta I_L = 20\text{mA} - 5\text{mA}$$

$$\Delta V_o = 33.211\text{mV} \quad V_o = 10\text{V}$$

$$\Delta = \underline{3.3211\%}$$

⑩ Max power in Zener diode

$$I_R = \frac{V^+ - V_Z}{R}$$

$$V_Z = V_{Z0} + r_Z I_Z$$

$$V_Z = 9.55\text{V} + 18 \left(\frac{25\text{V} - V_Z}{214.4} \right)$$

$$V_Z = 9.55\text{V} + 2.09888 - 0.0839V_Z$$

$$1.0839V_Z = 11.648806$$


$$V_Z = 10.7466\text{V}$$

$$I_Z = \frac{25 - 10.7466\text{V}}{214.4}$$

$$I_Z = 66.4802065\text{mA}$$

$$P_Z = I_Z V_Z = (66.480206\text{mA})(10.7466\text{V})$$

$$P_Z = 0.71443\text{W}$$

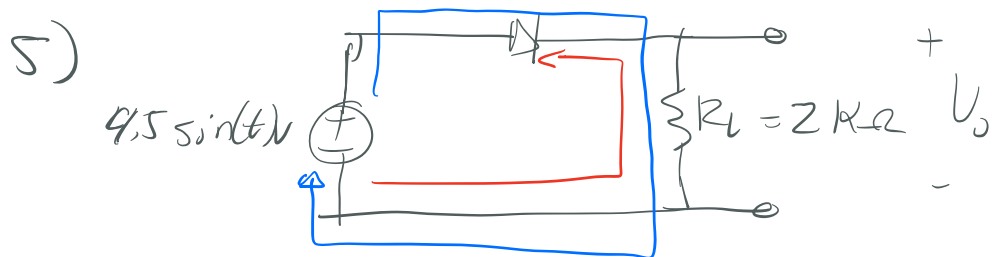

$V_D = 0.7V$ Find average value of V_o

⑪

$$V_o = V_s - 0.7V$$

$$V_o = 4.5 - 0.7V$$

$$\underline{V_o = 3.8V \text{ peak}}$$



$$V_o(\text{avg}) = \left(\frac{1}{T} \right) V_s(\text{max}) + \frac{V_D}{2}$$

$$V_o(\text{avg}) = \left(\frac{1}{T} \right) (4.5) + \frac{0.7}{2}$$

$$\underline{V_o(\text{avg}) = 1.08239V}$$

Correct

12

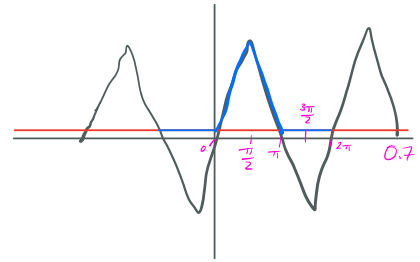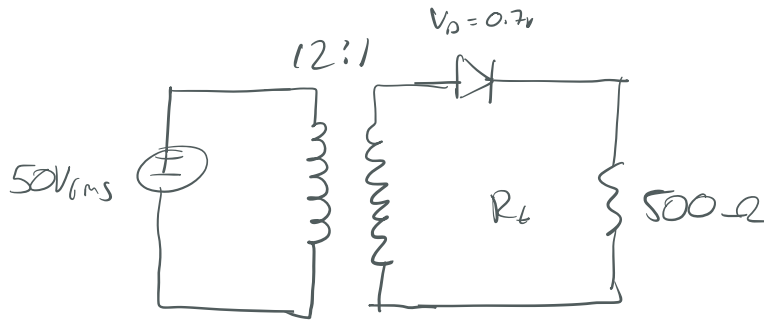

"For what fraction of a cycle does the diode conduct?"


$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

$$(\sqrt{2}) V_{rms} = V_p = 50 V_{rms} \sqrt{2} \Rightarrow V_p = 70.71\text{V}$$

$$V = \begin{cases} \text{triangle wave function, } 0 < t < \pi \\ 0.7 \dots \dots \dots \pi < t < 2\pi \end{cases}$$

c) proportioned conduction time = 46.06%

7)

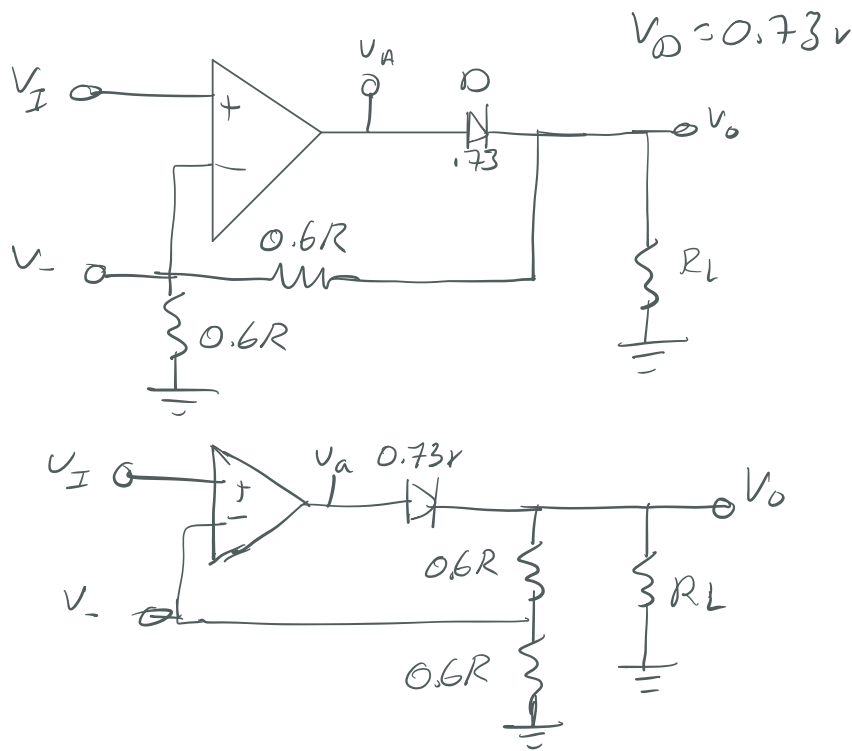

13

$$V_I = 1.5V$$

$$V_A = V_I \left(1 + \frac{R_F}{R_{in}} \right)$$

$$V_A = V_I (2)$$

$$V_A = 1.5(2) = \boxed{3V}$$

$$V_- = V_I = \boxed{1.5V}$$

$$V_O = V_A + 0.73$$


$$V_O = 3 - 0.73$$

$$\boxed{V_O = 3.73V}$$

$$2.27$$

$$V_- + V_A + V_O = 1.5 + 3 + 2.27 = \boxed{3.77V} \quad h$$

19) $V_I = -4.3\text{V}$

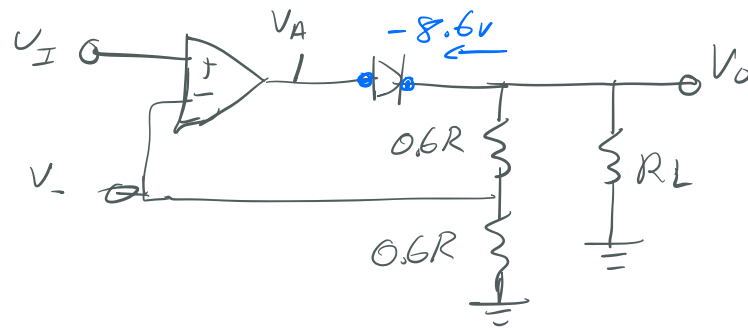

$$V_A = -4.3(2)$$

$$V_A = -8.6\text{V}$$

$$V_O = -8.6\text{V}$$

$$V_- = +4.3\text{V}$$

$$V_- + V_A + V_O = 4.3 - 8.6 - 8.6$$

$$= -12.9\text{V}$$

8)