

Emich HW2

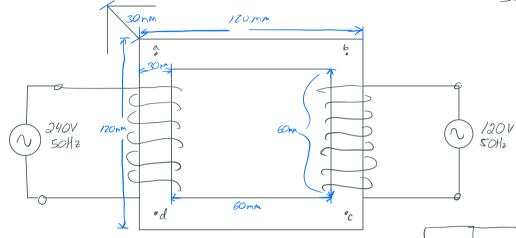

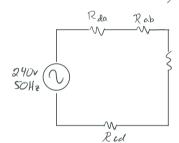

800:400 turns

a) Cou Reluctance, 11, =1500 11, = 477 1107



$$\begin{cases} R_{bc} & R_{t} = 4(R_{ab}) => 4(5.3051 \text{ K}) => \overline{R_{t}} = 212.206 \text{ K}\Omega \end{cases}$$

$$R_{ab} = \int_{M} \frac{90 \times 10^{-3}}{A} = \frac{(4\pi \times 10^{-7})(1500)(9 \times 10^{-9})}{(4\pi \times 10^{-7})(1500)(9 \times 10^{-9})} = \frac{R_{ab}}{R_{ab}} = 5.3057 \text{ K}\Omega$$

b)
$$l_m$$
 Refferred by prinary $\left(\frac{N_p^2}{R}\right)$

$$l_m = \frac{(800)^2}{712.706K}$$

$$\left[l_m = 3.0159 \text{ [H]}\right]$$

d)
$$I_{m}$$

$$I_{m} = \frac{V_{p}}{R_{c} || l_{m} l_{m}}$$

$$I_{m} = \frac{240}{947.487} = \sqrt{I_{m} - 253.303 \text{ mA}}$$

e)
$$\lambda = ?$$
 $\lambda_{p} = Li$
 $\lambda_{p} = (3.0159)(253.303 \text{ mA})$
 $\lambda_{p} = 0.7639 \text{ wb}$

$$\beta) \varphi = \frac{3}{R} = \frac{N_p I_n}{R}, \beta = \frac{1}{A}$$

$$\varphi = \frac{(800)(253.303 \text{ nA})}{212.20G \text{ K}\Omega} = 954.9796 \times 100 \text{ mb}$$