

Lab 3 Understanding Diodes

- Objective:
- verify diode signal circuits and to see the relationship between current voltage and switching frequency limitations
 - Matlab plots of generic diodes and P-N junction diodes & with addition of an LED
 - analyze AC resistances of diodes
 - different models
 - ~~@@~~ Oscilloscope set-up for V-I characteristics

Equipment

- Oscilloscope
- Power supply
- DMM bench-top
- DMM, handheld
- Function Generator
- ~~Power~~ Analog Discovery

Continued to page

SIGNATURE



DATE

2/15/22

DISCLOSED TO AND UNDERSTOOD BY

DATE

PROPRIETARY INFORMATION

TITLE

PROJECT

Continued from page

Components

- Resistors -


- 1K Ω
- 330 Ω
- 470 Ω
- 1M Ω

- Diodes -

- 1N914
- 1N3064
- 5V Zener (1N4733A or =)
- Red LED
- Green LED

Pre-Lab

- Use MATLAB for calculations

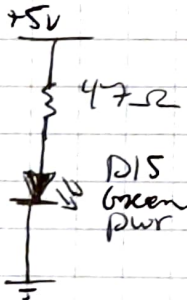

a) make the circuit w/ LED in backwards

b) Does it light? No, it does not

c) (Install it correctly) Does it light?
Yes, it does

d) The LED did not work in the reverse orientation because diodes have polarity, they only allow current through ~~in~~ in a certain direction

Continued to page

SIGNATURE

DATE

2/15/22

DISCLOSED TO AND UNDERSTOOD BY


DATE

PROPRIETARY INFORMATION

TITLE

PROJECT

Continued from page

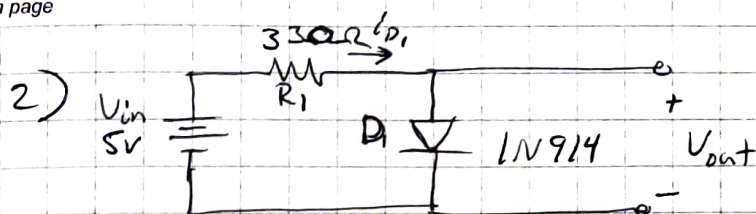

Diode forward $V = 1V$
 - forward $I = 300mA$

a) build the circuit

Calculate I_{R1} , V_{R1} , V_{out} when $V_{in} = 5V$

$$I_{R1} = \frac{5V}{330} = 15.1515 \text{ mA}$$

$$V_{R1} = 5V$$

$$V_o = 4.3V$$

$$V_o = V_{R1} - 0.7V$$

- when $V_{in} = 10V$

$$I_{R1} = \frac{10V}{330} = \cancel{303.03 \text{ mA}} \quad 30.303 \text{ mA}$$

$$V_{R1} = 10V$$

$$V_o = 7.3V$$

- when $V_{in} = 12V$

$$I_{R1} = \frac{12V}{330} = 36.363 \text{ mA}$$

$$V_{R1} = 12V$$

$$V_o = 11.3V$$

Continued to page


SIGNATURE

DATE

DISCLOSED TO AND UNDERSTOOD BY

DATE

PROPRIETARY INFORMATION

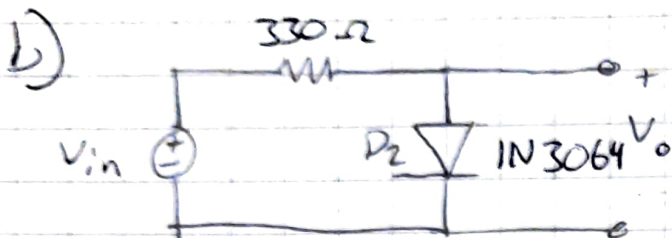

- when $V_{in} = 5V$

$$i_{D2} = \frac{5V}{330} = \underline{15.151 \text{ mA}}$$

$$V_{R1} = \underline{5V}$$

$$V_o = 5 - 0.7 = \underline{4.3V}$$

- when $V_{in} = 10V$

$$i_{D2} = \frac{10V}{330\Omega} = \underline{30.303 \text{ mA}}$$

$$V_{R1} = \underline{10V}$$


$$V_o = 10 - 0.7 = \underline{9.3V}$$

- when $V_{in} = 12V$

$$V_{R1} = \underline{12V}$$

$$i_{D2} = \frac{12V}{330} = \underline{36.363 \text{ mA}}$$

$$V_o = 12 - 0.7 = \underline{11.3V}$$

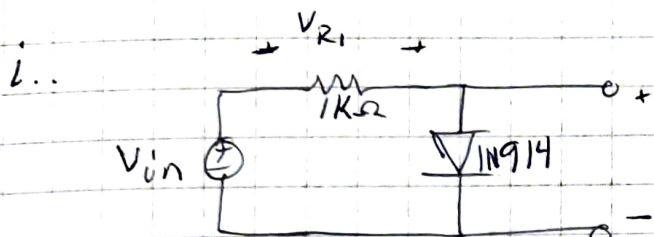

$V_{in} = 1 \text{ KHz Sine wave @ } 5 \text{ V}_{pp}$


$$I_{D1} = \frac{V_{R1}}{1K} = \frac{4.3V}{1K} = \underline{4.3 \text{ mA}}$$

$$V_{R1} = V_{in} - 0.7 = \underline{4.3 \text{ V}}$$

measured values

$$I_{D1} = \frac{4.3212}{1K} = \underline{4.3212 \text{ mA}}$$
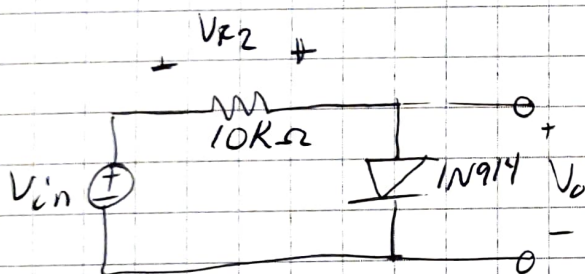
$$V_{R1} = \underline{4.312 \text{ V}} \quad \underline{4.3212 \text{ V}}$$



$V_{in} = 1 \text{ KHz Sine wave @ } 5 \text{ V}_{pp}$

	calculated	measured
I_{D2}	0.43 mA	4.4388 V
V_{R2}	4.3 V	0.44388 mA

- higher voltage due to larger resistor

$$I_{D2} = \frac{V_{R2}}{10K} = \frac{4.4388 \text{ V}}{10K}$$

$$I_{D2} = \frac{V_{R2}}{10K\Omega} = \frac{4.3}{10K\Omega} = \underline{0.43 \text{ mA}}$$

$$V_{R2} = V_{in} - 0.7 = \underline{4.3 \text{ V}}$$

Continued to page

SIGNATURE

Key...

DATE

2/28/22


DISCLOSED TO AND UNDERSTOOD BY

DATE


PROPRIETARY INFORMATION

Continued from page

c) D₁ Voltage plot

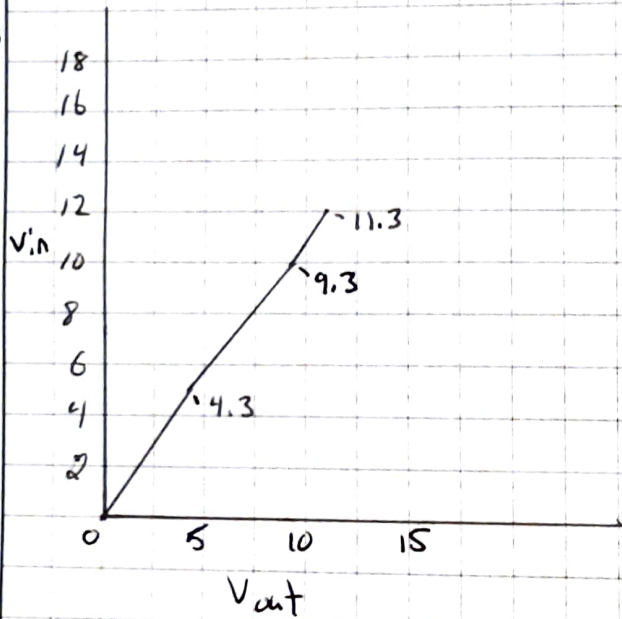


D₂ Voltage plot

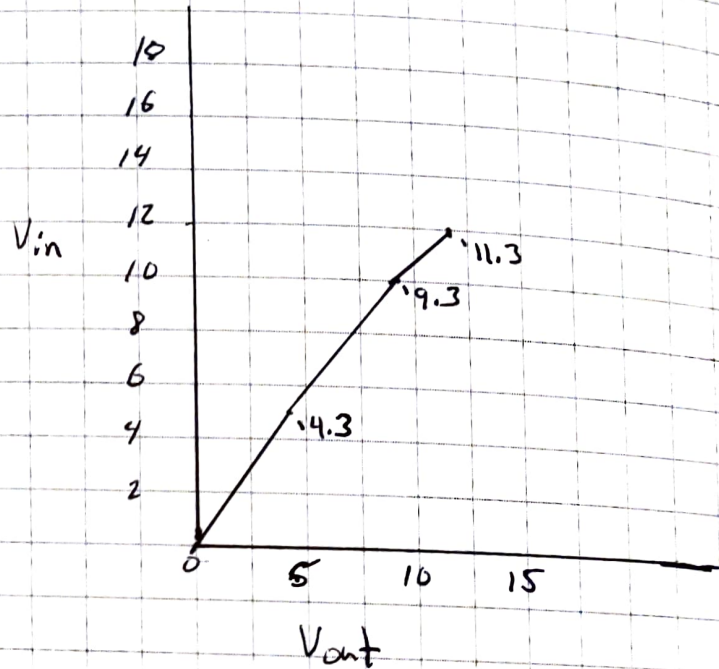


d)

D₁ 1N914

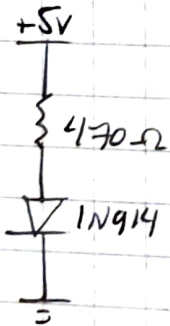

D₂ 1N3064

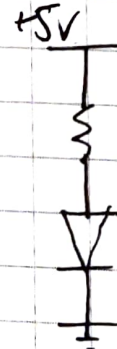

measured	datasheet value
0.7445V	1V max*

measured	Datasheet value
0.74120V	5V max*

V_{D1}

V_{D2}


* datasheet value is forward voltage and only the max value was given.

TITLE

PROJECT

Continued from page

di... missed that part.

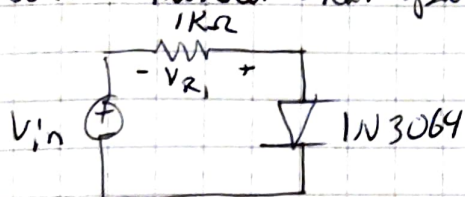


$$\text{calc } I_{D2} = \frac{V_{R1}}{10K\Omega}$$

$$= \frac{4.3}{10K}$$

$V_{in} = 1KHz \text{ sine @ } 5V_{p-p}$

measured V_{R1}	calculated	measured
V_{R1}	4.3v	4.3323v
i_{D2}	4.3mA	4.332mA

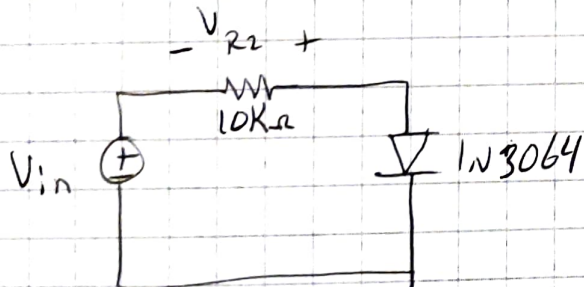$\frac{4.3323}{1K} \quad \frac{V_{in}}{1K\Omega}$
 forget I scratched that.



$V_{in} = 1KHz \text{ sine @ } 5V_{p-p}$

	calculated	measured
V_{R2}	4.3v	4.4424v
I_{D2}	0.43mA	0.442mA

$\frac{4.4424v}{10K\Omega}$

$$\text{calc } I_{D2} = \frac{V_{R2}}{10K\Omega}$$

$$= \frac{4.3v}{10K}$$

Continued to page

SIGNATURE

[Signature]

DATE

2/28/22

DISCLOSED TO AND UNDERSTOOD BY

DATE

PROPRIETARY INFORMATION