

Lat 2 pre-lab

- part of the pre-lab is to do all calculations of the lab. Tables of each section will be made now, then measured data will be filled in.


The purpose of this lab is to understand Operational Amplifier (OP-Amp) datasheets and to construct ~~four~~ four types of op-amp circuits

- 1) A Buffer
- 2) A Comparator
- 3) An inverting Op-Amp
- 4) A summing op-amp

Parameter	Specified Value			units
	min	Typical	Max	
Input offset voltage, V_{os}		5	10	mV
Input bias current, $I_{b/AE}$		50	200	pA
Input offset current, I_{os}		25	100	pA
CMRR	70	100		dB
Slew rate	8	13		V/ μ s

Tools


1) Buffer

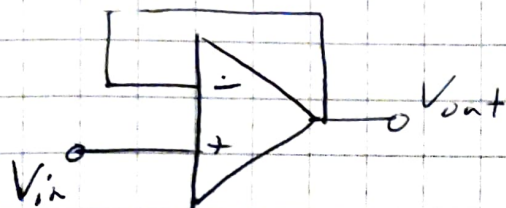

Vin (Volts)	Vout	
	Vout Calculated	Measured
+2.0	+2.0	
-2.0	-2.0	
5	5	
+7.0	+7.0	

$$V_{out} = V_{in}$$

2) Inverting OP-Amp

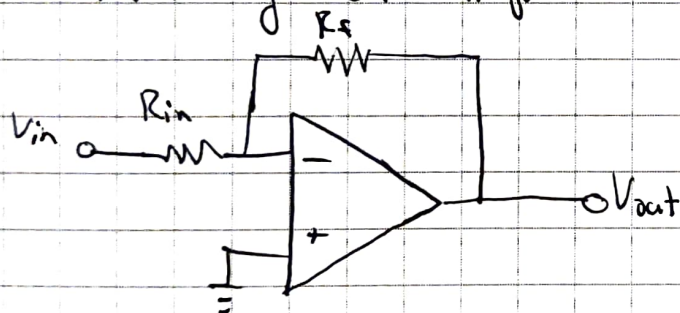

$$V_{out} = -\frac{V_{in}}{R_{in}} \cdot R_f$$

Vin (Volts)	Vout	
	Calculated	Measured
+0.2	0.001 -1	
-0.3	1.5	
0	0	
+0.32	-1.6	
+0.3	-2.4 -72	
-0.25	3.6 0.6	
-0.2	0.48	
+0.4	-3.84 -88	
	-0.96	

$$R_{in} = 2K\Omega$$

$$\rightarrow R_f = 10K\Omega$$

$$V_{out} = -V_{in} \left(\frac{10K\Omega}{2K\Omega} \right)$$

$$R_{in} = \cancel{2K\Omega} 10K\Omega$$


$$R_f = 24K\Omega$$

$$V_{out} = -V_{in} \left(\frac{24K\Omega}{\cancel{10K\Omega}} \right)$$

TITLE

Continued from page

3) Summing Amp

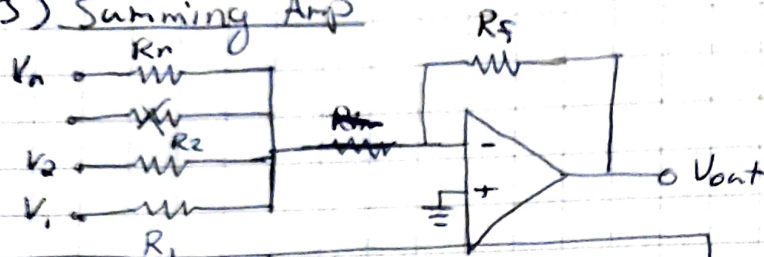

$$V_o = I_{Rf} \cdot R_f$$

$$R_1, R_2, R_n = 20 \text{ K}\Omega$$

$$I_{Rf} = \sum I_n$$

$$R_{f} = 20 \text{ K}\Omega$$

$$R_f = 20 \text{ K}\Omega$$

calc	Input V_o tags			V_{out}	
	V_1	V_2	V_3	calculated	measured
1	+1	+1	+1	3V	
2	-1	-1	+1	-1V	
3	-1	-1	+2	0 -1.8V	
4	+3	-3	-3	3V 3V 0	
5	-2	+1	-2	-3V	

$$1) I_{R_1} = \frac{1}{20\text{K}} = 0.05 \text{ mA}$$

$$I_{Rf} = 0.15 \text{ mA}$$

$$I_{R_2} = \frac{1}{20\text{K}} = 0.05 \text{ mA}$$

$$V_o = (0.15 \text{ mA})(20 \text{ K}\Omega) = 3 \text{ V}$$

$$I_{R_3} = \frac{1}{20\text{K}} = 0.05 \text{ mA}$$

$$2) I_{R_1} = \frac{-1}{20\text{K}} = -0.05 \text{ mA}$$

$$I_{Rf} = -0.05 \text{ mA}$$

$$I_{R_2} = \frac{1}{20\text{K}} = -0.05 \text{ mA}$$

$$V_o = (-0.05 \text{ mA})(20 \text{ K}\Omega) = -1 \text{ V}$$

$$I_{R_3} = \frac{+1}{20\text{K}} = 0.05 \text{ mA}$$

$$3) I_{R_1} = -\frac{1}{20\text{K}} = -0.05 \text{ mA}$$

$$I_{Rf} = -0.09 \text{ mA}$$

$$I_{R_2} = \frac{-1}{20\text{K}} = -0.05 \text{ mA}$$

$$V_o = (-0.09 \text{ mA})(20 \text{ K}\Omega) = -1.8 \text{ V}$$

$$I_{R_3} = \frac{2}{20\text{K}} = 0.1 \text{ mA}$$

Continued to page

SIGNATURE

DATE

DISCLOSED TO AND UNDERSTOOD BY

DATE

PROPRIETARY INFORMATION

4) $I_{R1} = \frac{3}{20K} = \cancel{0.15mA} \cdot 15mA$
 $I_{R2} = \frac{-3}{20K} = \cancel{-0.15mA} - 15mA$
 $I_{R3} = \frac{3}{20K} = \cancel{0.15mA} - 15mA$

$\cancel{I_{RF} = 0.015}$
 $I_{RF} = -0.15mA$


$V_o = (-0.15mA)(20K\Omega) = -3V$

5) $I_{R1} = \frac{-2}{20K} = \cancel{-0.01mA} 0.01mA$
 $I_{R2} = \frac{1}{20K} = 0.05mA$
 $I_{R3} = \frac{-2}{20K} = \cancel{-0.01mA} 0.01mA$

$I_{RF} = \cancel{0.03mA} - 0.15mA$

$V_o = (\cancel{0.03mA})(20K\Omega) = -3V$
 $-0.15mA$

4) Comparator

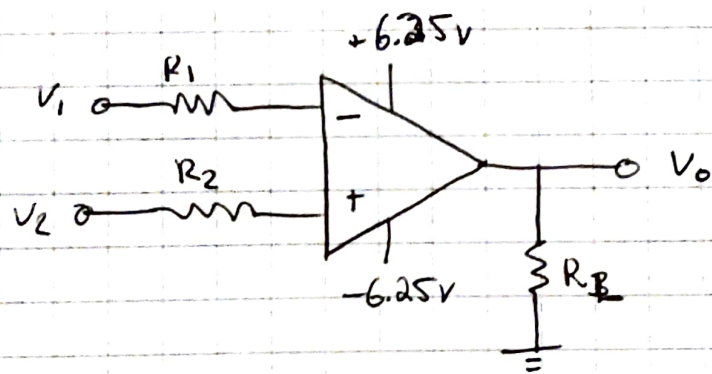

$R_1 = R_2 = 10K\Omega$
 $R_L = 10K\Omega$

Input		Output	
V_1	V_2	Calculated	measured
(-)	(+)		
+4	+1	-5V	
+2	+3	5V	
+1	0	-5V	
+4	+4	0	
0	+1	5V	
+3	+2	-5V	

- 1/5/24
- If $(-) > (+)$; $V_o = -5V$
 - If $(-) < (+)$; $V_o = 5V$
 - If both the same, $V_o = 0V$